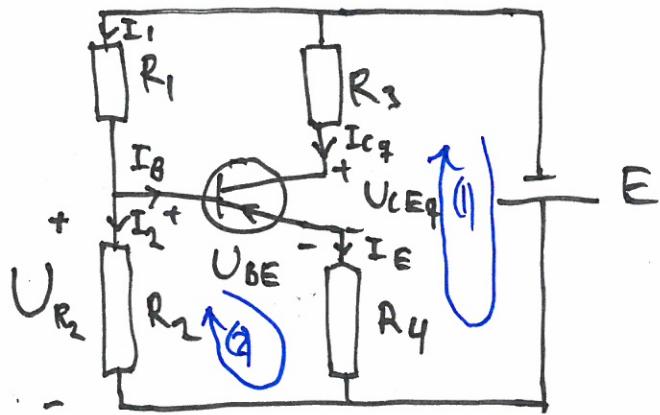


E-4) Låkströmschema:



$$I_{CQ} = -3.0 \text{ mA}$$

$$U_{CEQ} = -5.0 \text{ V}$$

$$R_1 = 18 \text{ k}\Omega$$

$$R_4 = 1.6 \text{ k}\Omega$$

$$E = 12 \text{ V}$$

Ur datablad $\Rightarrow h_{FE} = 140, U_{BE} = -0.65 \text{ V}$

$$(1) E + I_E \cdot R_4 + U_{CEQ} + I_{CQ} \cdot R_3 = 0$$

$$(2) -I_E \cdot R_4 + U_{R2} - U_{BE} = 0$$

$$(3) I_E = I_c + I_B$$

$$(4) I_B = I_c / h_{FE}$$

$$(4) \Rightarrow I_B = \frac{-3.0}{140} \approx -21 \mu\text{A}$$

$$(3) \Rightarrow I_E = -3 \text{ mA} - 21 \mu\text{A} \approx -3 \text{ mA} (\approx I_{CQ})$$

$$(1) \Rightarrow R_3 = \frac{-E - U_{CE} - I_E \cdot R_4}{I_{CQ}} = \frac{-12 + 5 - 3 \text{ mA} \cdot 1.6 \text{ k}\Omega}{-3 \text{ mA}} \approx 733 \Omega$$

$$(2) \Rightarrow U_{R2} = U_{BE} + I_E \cdot R_4 = -0.65 - 3 \text{ mA} \cdot 1.6 \text{ k}\Omega \\ = -5.45 \text{ V}$$

$$R_3 = 733 \Omega$$

$$I_2 = I_1 - I_B = \frac{-E - U_{R2}}{R_1} - I_B = \frac{-12 + 5.45}{18 \text{ k}\Omega} - 21 \mu\text{A} = -342 \mu\text{A}$$

$$R_2 = \frac{U_{R2}}{I_2} = \frac{-5.45}{-342 \mu\text{A}} \approx 15.9 \text{ k}\Omega$$

$$R_2 = 15.9 \text{ k}\Omega$$