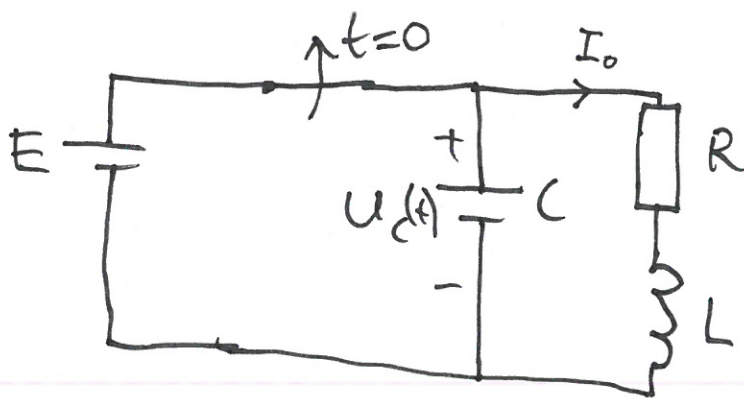


C-6)



$$R = 20 \Omega, L = 5.0 \text{ H}$$


$$C = 25 \text{ mF}$$

$$E = 10 \text{ V}$$

$$u_c(t) = E \quad \text{for } t < 0$$

$$I_0 = E/R \Rightarrow I_0 = 0.5 \text{ A}$$

Operator schema:

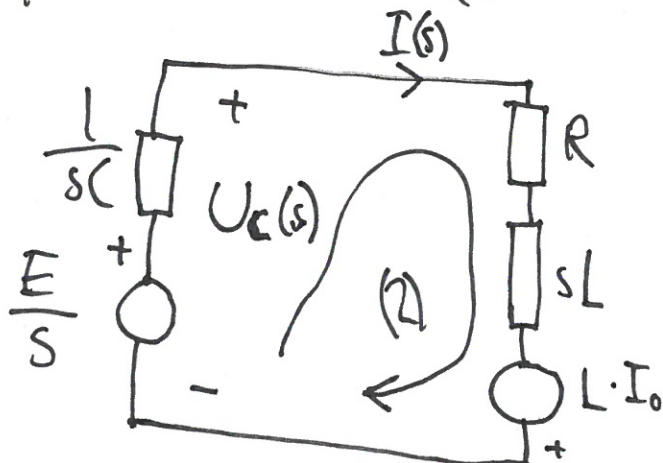

$$(1): U_c(s) = -\frac{1}{sC} \cdot I(s) + \frac{E}{s}$$

$$(2): \frac{E}{s} - \frac{1}{sC} \cdot I(s) - R \cdot I(s) - sL \cdot I(s) + L \cdot I_0 = 0$$

$$(2) \Rightarrow I(s) = \frac{\frac{E}{s} + L \cdot I_0}{R + sL + \frac{1}{sC}}$$

$$(2) \Rightarrow I(s) \text{ insatt i (1)} \Rightarrow$$

$$\begin{aligned} U_c(s) &= \frac{E}{s} - \frac{1}{sC} \cdot \frac{\frac{E}{s} + L \cdot I_0}{R + sL + \frac{1}{sC}} \\ &= \frac{10}{s} - \frac{1}{s \cdot 0.025} \cdot \frac{\frac{10}{s} + 5 \cdot 0.5}{20 + 5 \cdot s + \frac{1}{s \cdot 0.025}} \\ &= \frac{10}{s} - \frac{\frac{10}{s} + 2.5}{0.5s + 0.125s^2 + 1} = \frac{10}{s} - \frac{10 + 2.5s}{0.125s \cdot (s^2 + 4s + 8)} \\ &= \frac{10 \cdot 0.125 \cdot (s^2 + 4s + 8) - 10 - 2.5s}{s \cdot 0.125 \cdot (s^2 + 4s + 8)} \\ &= \frac{1.25s^2 + 5s + 10 - 10 - 2.5s}{0.125s \cdot (s^2 + 4s + 8)} = \frac{1.25s^2 + 2.5s}{0.125s \cdot (s^2 + 4s + 8)} \\ &= \frac{10s + 20}{s^2 + 4s + 8} = \frac{10 \cdot (s+2)}{s^2 + 4s + 2^2 - 2^2 + 8} = \frac{10 \cdot (s+2)}{(s+2)^2 + 2^2} \end{aligned}$$

Parlören \Rightarrow

$$u_c(t) = 10 \cdot e^{-2t} \cdot \cos(2t) \text{ V} \quad t > 0$$