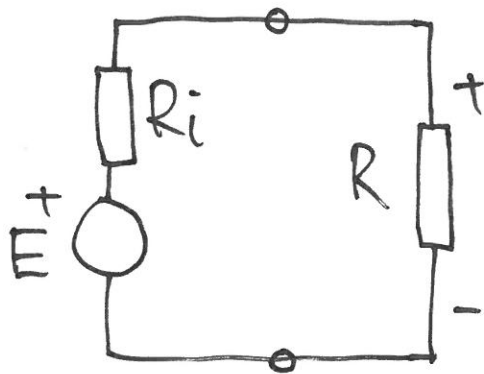


1-15)



$$R_i = 0,10 \Omega$$

$$R = 1,0 \text{ k}\Omega$$

$$U = 2,04$$

Spänningsdelning:

$$U = \frac{R \cdot E}{R + R_i} \Leftrightarrow U \cdot (R + R_i) = R \cdot E \Leftrightarrow$$

$$E = \frac{U \cdot (R + R_i)}{R} = \frac{2,04 \cdot (1,0 \text{ k} + 0,10)}{1,0 \text{ k}}$$

$$= 2,040204 \text{ V}$$

$$\text{Felet är } |U - E| = 2,04 \cdot 10^{-4} \approx 0,2 \text{ mV}$$