
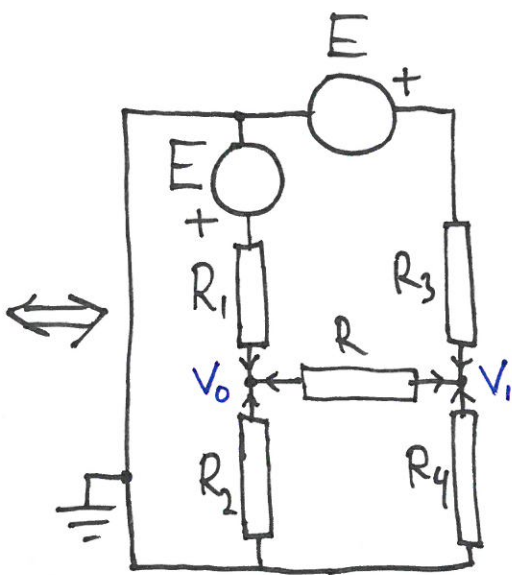


1.24 b)

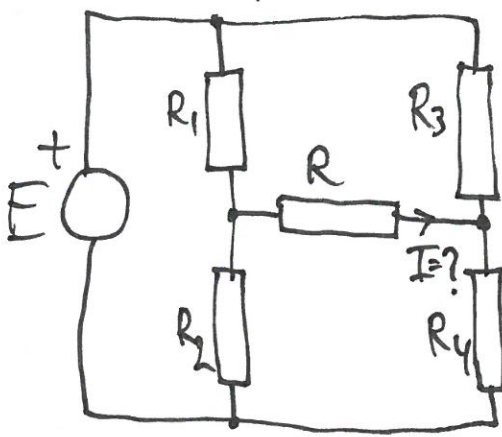

$$E = 6 \text{ V}$$

$$R_1 = 1 \Omega$$

$$R_2 = 5 \Omega$$

$$R_3 = 2 \Omega$$

$$R_4 = 4 \Omega$$

$$R = 3 \Omega$$

$$\begin{cases} \frac{0 - V_0}{R_2} + \frac{E - V_0}{R_1} + \frac{V_1 - V_0}{R} = 0 \end{cases}$$

$$\begin{cases} \frac{V_0 - V_1}{R} + \frac{E - V_1}{R_3} + \frac{0 - V_1}{R_4} = 0 \end{cases}$$

$$\begin{cases} -\left(\frac{1}{R} + \frac{1}{R_1} + \frac{1}{R_2}\right) \cdot V_0 + \frac{1}{R} \cdot V_1 = \frac{-E}{R_1} \\ \frac{1}{R} \cdot V_0 - \left(\frac{1}{R} + \frac{1}{R_3} + \frac{1}{R_4}\right) \cdot V_1 = \frac{-E}{R_3} \end{cases}$$

$$\begin{cases} -\left(\frac{1}{3} + \frac{1}{1} + \frac{1}{5}\right) \cdot V_0 + \frac{1}{3} \cdot V_1 = \frac{-6}{1} \\ \frac{1}{3} \cdot V_0 - \left(\frac{1}{3} + \frac{1}{2} + \frac{1}{4}\right) \cdot V_1 = \frac{-6}{2} \end{cases} \Leftrightarrow \begin{cases} -\frac{23}{15} \cdot V_0 + \frac{1}{3} \cdot V_1 = -6 \quad (1) \\ \frac{1}{3} \cdot V_0 - \frac{13}{12} \cdot V_1 = -3 \quad (2) \end{cases}$$

$$(2) \Rightarrow V_0 = -9 + \frac{13}{4} \cdot V_1 \quad (*)$$

(*) insatt i (1) ger:

$$-\frac{23}{15} \cdot \left(-9 + \frac{13}{4} \cdot V_1\right) + \frac{1}{3} \cdot V_1 = -6 \Leftrightarrow \frac{69}{5} + \left(\frac{1}{3} - \frac{23 \cdot 13}{15 \cdot 4}\right) \cdot V_1 = -6 \Leftrightarrow$$

$$\frac{20 - 299}{60} \cdot V_1 = \frac{-30 - 69}{5} = \frac{-99}{5} \Leftrightarrow V_1 = \frac{-99 \cdot 60}{5 \cdot -279} = \frac{-9 \cdot 11 \cdot 5 \cdot 12}{5 \cdot -9 \cdot 31} = \frac{132}{31} \text{ V}$$

$$(*) = -9 + \frac{13}{4} \cdot \frac{132}{31} = \frac{-31 \cdot 9}{31} + \frac{13 \cdot 11 \cdot 4 \cdot 3}{4 \cdot 31} = \frac{-279 + 429}{31} = \frac{150}{31}$$

$$I = \frac{V_0 - V_1}{R} = \frac{\frac{150}{31} - \frac{132}{31}}{3} = \frac{6}{31} \approx 0.19 \text{ A}$$

$$I \approx 0.19 \text{ A}$$