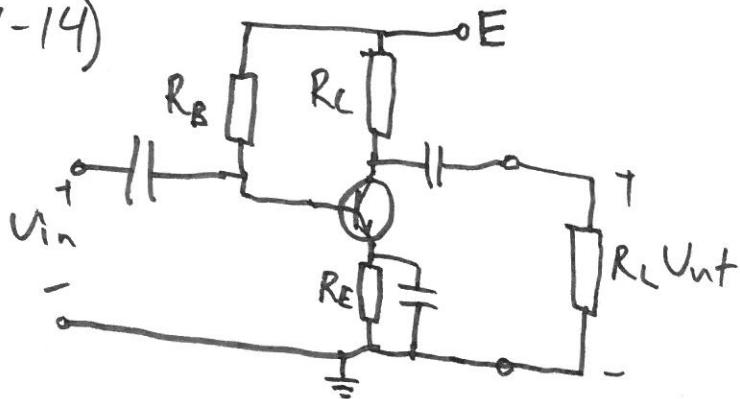


4-14)



$$R_B = 560 \text{ k}\Omega$$

$$R_c = 2 \text{ k}\Omega$$

$$R_E = 1 \text{ k}\Omega$$

$$R_L = 2 \text{ k}\Omega$$


$$h_{11} = 2 \text{ k}\Omega$$

$$h_{12} = 2 \cdot 10^{-4}$$

$$h_{22} = 50 \mu\Omega^{-1}$$

$$h_{21} = 300$$

äquivalent smäsignalschema:

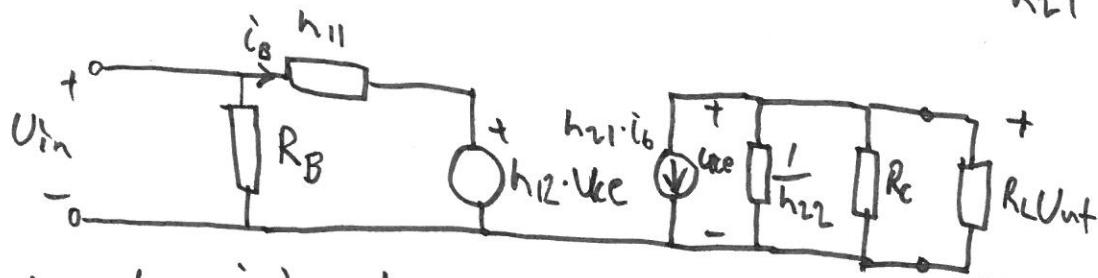

stegets inimpedans:

$$Z_{in} = R_B // h_{11} \approx h_{11} \quad (\text{da } R_B \gg h_{11}) = 2 \text{ k}\Omega$$

stegets utimpedans:

$$Z_{out} = \frac{1}{h_{22}} // R_C = 1.8 \text{ k}\Omega$$

stegets spänningsförstärkning:

$$(1) U_{in} = h_{11} \cdot i_B + h_{21} \cdot V_{ce}$$

$$(2) V_{out} = -h_{21} \cdot i_B \cdot Z_{out} // R_L$$

Vout = Vce & (2) i (1) ger:

$$(3) U_{in} = h_{11} \cdot i_B - h_{12} \cdot h_{21} \cdot i_B \cdot Z_{out} // R_L$$

$$F = \frac{V_{out}}{U_{in}} = \frac{-h_{21} \cdot i_B \cdot Z_{out} // R_L}{h_{11} \cdot i_B - h_{12} \cdot h_{21} \cdot i_B \cdot Z_{out} // R_L} = \frac{-h_{21} \cdot Z_{out} // R_L}{h_{11} - h_{12} \cdot h_{21} \cdot Z_{out} // R_L} = \frac{1}{h_{11} - h_{12} \cdot h_{21} \cdot Z_{out} // R_L} =$$

$$= -147 \text{ ggr}$$