

9. WAVE ACTIVE FILTERS

9.1

Determine first the \mathbb{K} matrix for a shunt admittance. We get

$$V_1 = V_2$$

$$Y_1 = Y(G_1 - I_2)$$

i.e., $\mathbf{K} = \begin{pmatrix} 1 & 0 \\ Y & 1 \end{pmatrix}$. Inserting $A = 1$, $B = 0$, $C = Y$ and $D = 1$ into Eq. (9.19) yields

$$s_{11} = (1 - YR - 1)/\Delta$$

$$s_{12} = 2R/G_2/\Delta$$

$$s_{21} = 2/\Delta$$

$$s_{22} = -(1 + YR_1 - R_1G_2)/\Delta$$

$$\Delta = 1 + YR_1 + R_1G_2$$

After simplification we get

$$s_{11} = (G_1 - G_2 - Y)(G_1 + G_2 + Y)$$

$$s_{12} = 2G_2/(G_1 + G_2 + Y)$$

$$s_{21} = 2G_1/(G_1 + G_2 + Y)$$

$$s_{22} = (G_2 - G_1 - Y)(G_1 + G_2 + Y)$$

$$s_{11} = -Y/(2G + Y)$$

$$s_{12} = 2G/(2G + Y)$$

$$s_{21} = 2G/(2G + Y)$$

$$s_{22} = -Y/(2G + Y)$$

Alternatively, the scattering matrix for a series impedance Z is according to Eq. (9.20)

$\mathbf{S} = \frac{1}{Z + 2R} \begin{pmatrix} Z, 2R \\ 2R, Z \end{pmatrix}$ using the theorem with a series impedance embedded between two gyrators. We get a shunt admittance $Y = Z/R^2$. Hence, a series impedance with $Z = YR^2$ yields

$$\mathbf{S} = \frac{1}{Y + 2G} \begin{bmatrix} Y & 2G \\ 2G & Y \end{bmatrix}$$

The gyrators correspond, according to Figure 9.9, to sign-inversion of the reflected waves. Hence we change the signs of the factor that is multiplied with A_2 . The scattering matrix for a gyrator is

$$\begin{bmatrix} B_1 \\ B_2 \end{bmatrix} = \begin{bmatrix} 0 & -1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} A_1 \\ A_2 \end{bmatrix}. \text{ We get the scattering matrix for an embedded two-port}$$

$$\begin{bmatrix} B_1 \\ B_2 \end{bmatrix} = \begin{bmatrix} 0 & -1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} s_{11} & s_{12} \\ s_{21} & s_{22} \end{bmatrix} \begin{bmatrix} 0 & -1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} -s_{21} & -s_{22} \\ s_{11} & s_{12} \end{bmatrix} \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} \text{ and with the series}$$

$$\text{impedance } Z = YR^2 \text{ we get } \mathbf{S}_Y = \frac{1}{Y + 2G} \begin{bmatrix} -Y & 2G \\ 2G & -Y \end{bmatrix}$$

9.2

We have the incident and reflected waves to a port $a = v + R_i$ and $b = v - R_i$ where all variables are sinusoidal. This yields $V = (a + b)$ and $I = (a - b)/R$ where V and I are r.m.s. values.

The power into a port is: $P = \text{real}\{VI^*\} = (a + b)(a - b)/R = (|a|^2 - |b|^2)/R = G(|a|^2 - |b|^2)$

9.3

We get

$$L_1' = 2R_0\tau_5 \quad C_1' = \tau_6/(2R_0)$$

$$L_2' = R_0\tau_3/2 \quad C_2' = 2\tau_4/R_0$$

$$L_3' = 2R_0\tau_2 \quad C_3' = \tau_1/(2R_0)$$


and

$$\tau_1 = 2\Omega_2/\omega^2 L_3 \quad \tau_4 = C_2/2\Omega_2$$

$$\tau_2 = L_3/2\Omega_2 \quad \tau_5 = L_1/2\Omega_2$$


$$\tau_3 = 2\Omega_2/\omega^2 C_2 \quad \tau_6 = 2\Omega_2/\omega^2 L_3$$

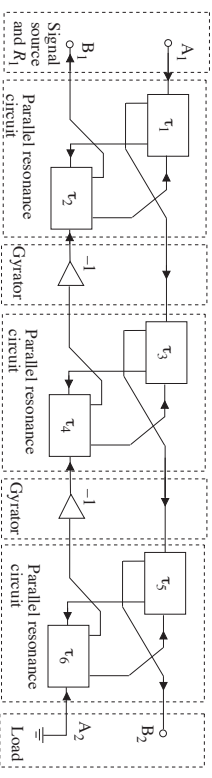The constant $R_0 > 0$ is arbitrary and affects only the impedance level in the wave two-ports.



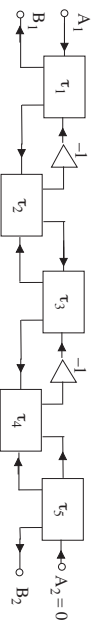9.4

A crossover network has not very high stopband attenuation in the two stopbands. Hence, we may realize a lowpass filter and use to complementary output for the highpass part. We get



where the inductances and yield the τ -factors $\tau_1 = L/2R$ and $\tau_5 = RC/2$, respectively.

9.5

9.6

According to Fel'dkellers Eq. (9.37) we have: $|s_{11}|^2 + |s_{21}|^2 = 1$

In this case, we estimate that $|s_{11}| \leq 20$ dB in the passband, i.e., the maximum of the magnitude of reflection function is less than $|s_{11}| = 10^{-\text{Attmax} \times 1/20} = 10^{-(20/20)} = 0.1$ and

$$|s_{21}| = \sqrt{1 - |s_{11}|^2} = 0.994987 \Rightarrow \text{Attmax} = 0.043648 \text{ dB}$$