

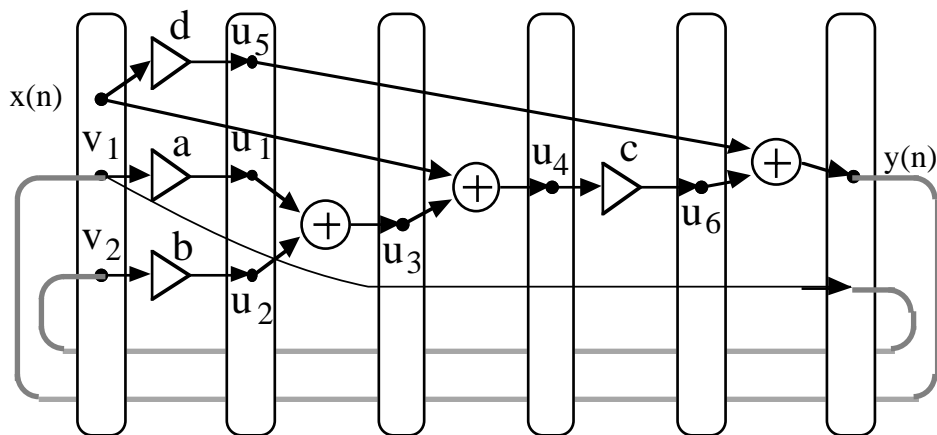


7.19 a) Assign names to all nodes.

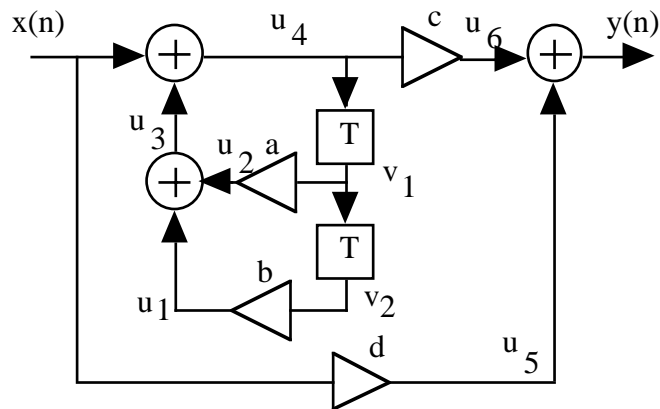

- b)
- |                      |                                     |
|----------------------|-------------------------------------|
| $u_1 := a v_1(n)$    | Which can be simplified to          |
| $u_2 := b v_2(n)$    | $u_4 := x(n) + a v_1(n) + b v_2(n)$ |
| $u_5 := d x(n)$      | $y(n) := d x(n) + c u_4$            |
| $u_3 := u_1 + u_2$   | $v_2(n+1) := v_1(n)$                |
| $u_4 := x(n) + u_3$  | $v_1(n+1) := u_4$                   |
| $u_6 := c u_4$       |                                     |
| $y(n) := u_5 + u_6$  |                                     |
| $v_2(n+1) := v_1(n)$ |                                     |
| $v_1(n+1) := x(n)$   |                                     |

c)

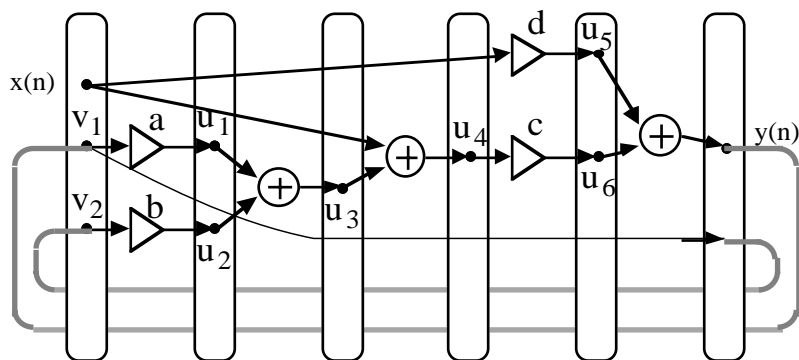

In Fig. 7.19d the operations are drawn modulo  $T_{min}$ , in this case modulo 8.

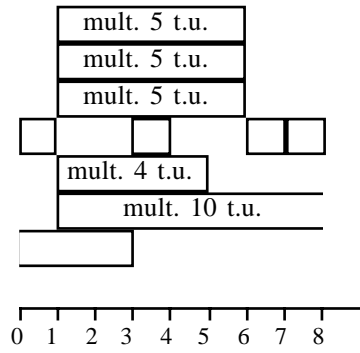


Fig. 7.19d. Timing diagram of schedule.

"I will eat your textbook for only 125 Swedish kronas"